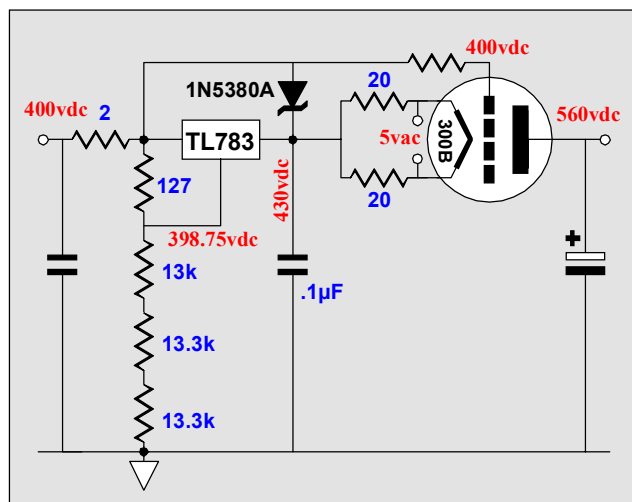




and dividing it by 0.0047. For example, if the cathode-to-plate voltage is 150 volts and the total idle current draw through the 300B is 105 mA (the cascode's current draw must be added), then the 300B needs to see -12.5 volts, thus Ra must equal  $12.5/0.0047 = 2660$  ohms. The best move would be to replace the plate resistor Ra with a constant current source, as a current source will help realize much more gain. A tube current source is not possible here, but a FET current source such as the 1N5314 or CRO-470 will work well.

Since adding a solid-state current source has cracked the hybrid door ajar, let's swing it wide open. Texas Instruments makes a great little three pin adjustable regulator with a 125 volt input-to-output voltage limit, the TL783, which houses a MOSFET pass device. Using this regulator in series with the 300B gives us the best of both technologies, the TL783 is quiet and accurate and the 300B is high-voltage tough. The principle of operation is simple enough. The 3 pin regulator strives to maintain a constant voltage output by increase and decrease its conduction. As the TL783 responds to voltage fluctuations at its output, the 300B sees a varying cathode-to-grid voltage, which allows the 300B to track the IC regulator.




The zener provides a discharge path for the output capacitor and a means of protecting the IC in the event of an over-voltage from short-circuits and a blown fuse.

One problem with this circuit is the input-to-output dropout voltage limit for the IC regulator. In order for TL783 to work, it needs to see at least 10 volts across its leads at 100 mA of current draw. This means that the 300B's grid can only get to within -10 volt of its cathode, which will impose a dropout voltage of 125vdc. Not that much headroom, in other words. Only a 5% drop in the 560 volt power supply can be allowed before the regulator starts to complain. Of course, the lower the total current passed, the smaller the dropout voltage. For example, at 50 mA, the raw power supply can drop 11%, without the regulator falling out of regulation. Still the -10 volt grid voltage sets limit.

The solution is to pre-bias the grid positively so that a 0 volt or even a positive grid voltage is possible. The circuit below shows one way to achieve this end.

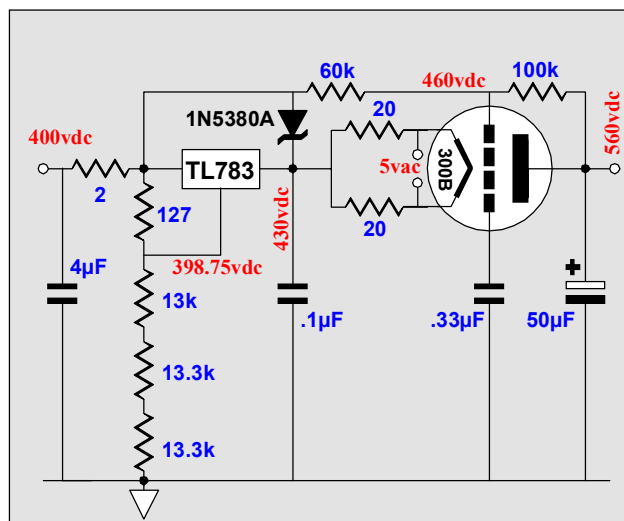
Now the raw power supply voltage can drop 20% from its nominal 560vdc value and the regulator will still maintain regulation.



For greater than 100 mA loads, the 60k resistor that connects to the 300B's grid can be replaced with a 20 volt zener; the .33 capacitor is removed; and the 100k resistor is replaced with a high wattage 1k resistor. This setup delivers the bulk of the output current from the zener and the 1k resistor's path. The 300B handles the difference. Such a only works well when the load current never drops below a threshold value; in this case, it is about 130 mA.

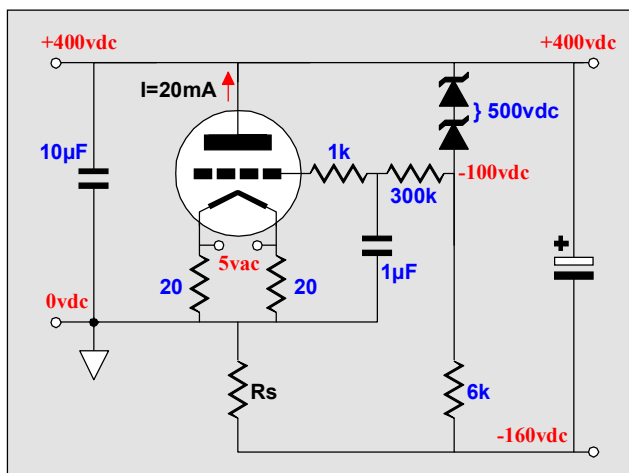
## Shunt 300B Regulators

All the advantages that the 300B brought to the series regulator it also brings to the shunt regulator. The shunt regulator works best with load currents that remain mostly fixed, such as single-ended amplifiers and push-pull Class-A amplifiers. The problem the shunt pass device faces is that it must see the whole voltage differential that the load sees. This will greatly decrease the maximum cathode current the 300B can draw. Given the 40 watt dissipation and a 400 volt cathode-to-plate voltage, the maximum current is 100 mA. This 100 mA limit is not maximum idle current. 50 mA is closer to the real maximum idle current, as the shunt pass device must vary its conduction through the series resistor is what makes the shunt regulator to work.




The circuit above is an example of an inverted shunt regulator. The zener works as the voltage reference. The 300B's transconductance provides the feedback mechanism to maintain the output voltage. Unfortunately, the regulator is poor due to the 300B limited transconductance.

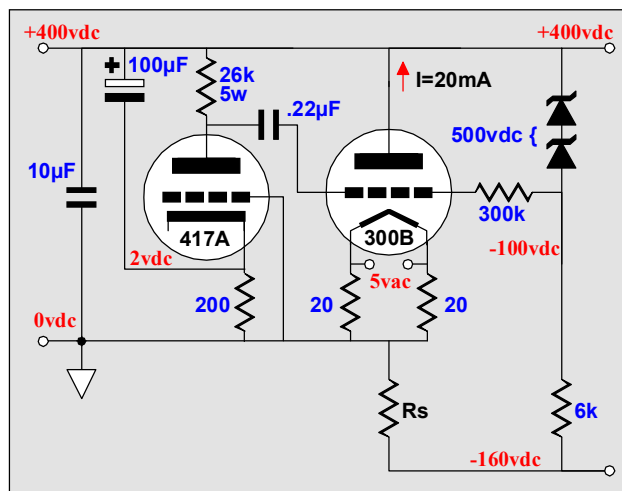Improving the regulation requires more gain, which the 417A provides plentifully, in the following circuit. The 100 µF capacitor relays deviations at the output to the cathode of the 417A, which is then in phase amplified at its plate. The plate's connection to the 300B's grid via the coupling capacitor is what drives this regulator.




Taking the hybrid route is tougher to accomplish than it was in the series regulator. Because of the high idle current, the TL431, the obvious choice, is not useable.

(One trick might be to use the TL783 in an wildly different configuration. I have not actually built this shunt regulator, so no guarantees are offered. But the premise seems reasonable enough: the TL783 is controlling the current through the 300B. If the output voltage climbs higher than 400 volts, the TL783's adjustment pin sees a voltage closer to its output pin's voltage. As far as the TL783 is concerned, the output voltage is collapsing so it increases its conduction to compensate for the dropping output voltage. This increased conduction will increase the voltage drop across the shunt resistor Rs and bring down the voltage.)

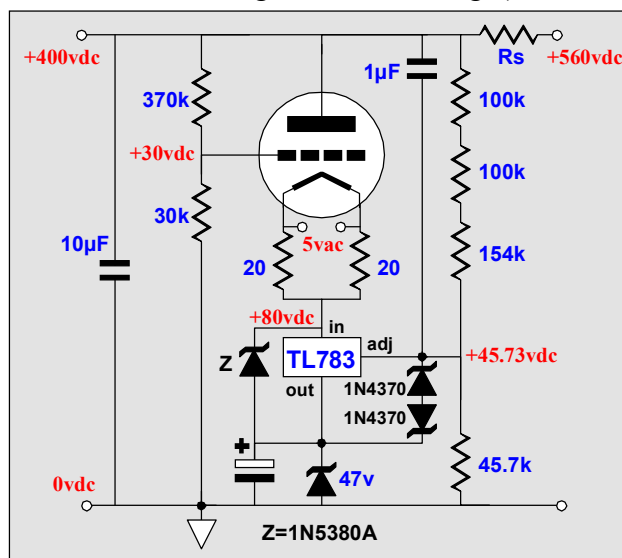
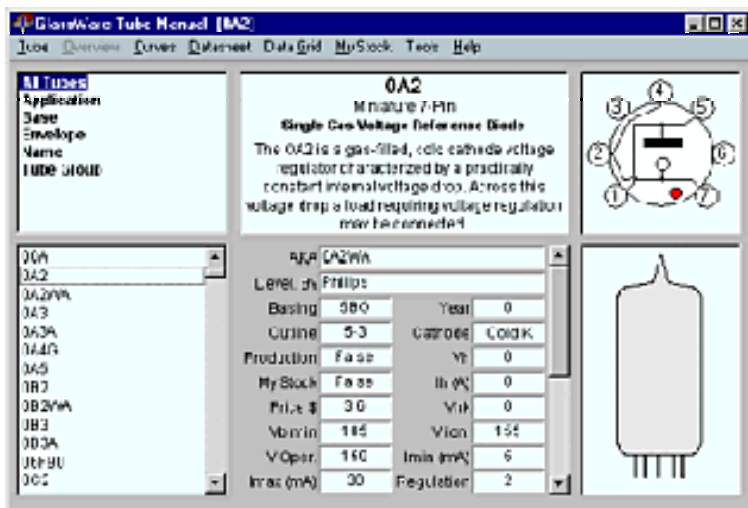
# GLASSWARE TUBE MANUAL

A true 32-bit Windows program, GlassWare Tube Manual is both user friendly and powerful. It's all here: plate curves, mu, rp, Gm, Vh, Ih, base and outline schematics, and essential characteristics for many of the tubes. Powerful search and filtering tools give control over this tube manual's large library of tubes (11,000). Look up your favorite tubes (6SN7, KT88, 2A3, and 6922) and discover other great tubes you didn't know existed. With the aid of easy-to-use editing tools, tubes can be added or subtracted to the database. Keep track of your own tube collection with your personal tube database. Like all GlassWare programs, GlassWare Tube Manual allows you to print the results. Hard copies of all the tubes in in this tube manual are a button click away. And tube substitutions are given for over 2000 tube types.



Click on image to see enlargement

Windows 95 / 98 / Me / NT

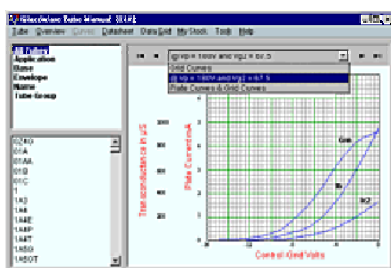



Plate Curves

Datasheets


| Name | Count | Brand               | Condition | Comments                   |
|------|-------|---------------------|-----------|----------------------------|
| 6X4  | 52    | Amperex             | NOS       | Good parts                 |
| 6X4T | 7     | Amperex             | New       |                            |
| 6X4T | 2     | GE                  | NOS       | Worth their weight in gold |
| 6X4T | 2     | Chatham Electronics | Used      |                            |
| 6X4T | 1     | GE                  | Used      | Short leads                |
| 6X4T | 1     | GE                  | NOS       |                            |
| 6X4T | 3     | Mullard             | NOS       | Gold pins, 1963            |
| 6X4T | 2     | RCA                 | Used      | Test strong                |
| 6X4T | 4     | RCA                 | New       | Sell at Flea Market        |
| 6X4T | 14    | Tung Sol            | NOS       | New looking box of         |

User's own stock DB

Tube Substitutions

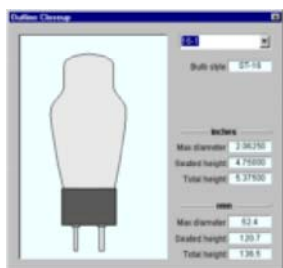


Tube Outlines

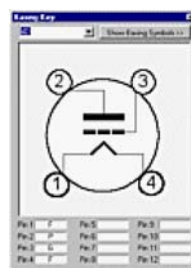

Tube Basing

Complex DB Filtering

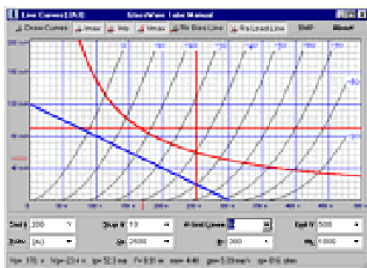

Live Curves for over 40 tubes

Database editor

For more information, please visit our Web site or write us at:

## GLASSWARE

PO Box 2

Santa Cruz CA 95063 USA

[www.glass-ware.com](http://www.glass-ware.com)

(Should the output voltage drop instead, the TL783's conduction eases up and the regulator's output voltage climbs with the decreased voltage drop across resistor Rs.)

(The output of the TL783 cannot be sent directly ground, as the adjustment pin must see a voltage 1.27 volts lower than its output. Thus the role of the 47 volt zener. It brings the TL783's output up to 47 volts above ground. A further advantage to using the zener is that it allows for higher voltage dropping resistors that relay the regulator's output voltage to the adjustment pin. The two 1N4370 zeners are there to protect the TL783's adjustment pin from high-voltage spikes.

The 1µF capacitor might not be a good idea, as the zeners might prove too slow to save the TL783. Actually, in this circuit and all the other hybrid regulators, avoid over designing. For example, do not eliminate the 2 ohm resistor at the output or decide to shunt the adjustment pin to ground in the series regulators by adding a capacitor. High-voltages kill solid-state devices easily.

### Conclusion

The 300B has a potentially wider use than just a single-ended output tube. High-voltage regulator pass device is just one possibility.

Of course other tubes could be used, such as a triode connected 6550. But having a 300B based regulator would be just too delicious to pass up.

If anyone tries any of these circuits, please send the results in to share with all of us.

//JRB

**goldpoint™**

**Your Volume Control makes a difference.**

Low Noise · 24 Position Stepped Attenuator  
Precision Control · Long Lasting Contacts  
10K - 25K - 50K - 100K - 250K

**Arn Roatcap, Inc.**  
1248 Valerian Court #4 Phone: (408) 737-3920  
Sunnyvale, CA 94086-9155 E-mail: [info@goldpt.com](mailto:info@goldpt.com)

<http://www.goldpt.com>